

PANIC ALARM

4 Zone Alarm System


TECHNICAL NOTE

**Applications guide to provide common
sounders when two ore more panels are
connected together**

Pt. No. 600 - 110 (Panic Alarm Control Panel)

© 2007

Connection Diagram

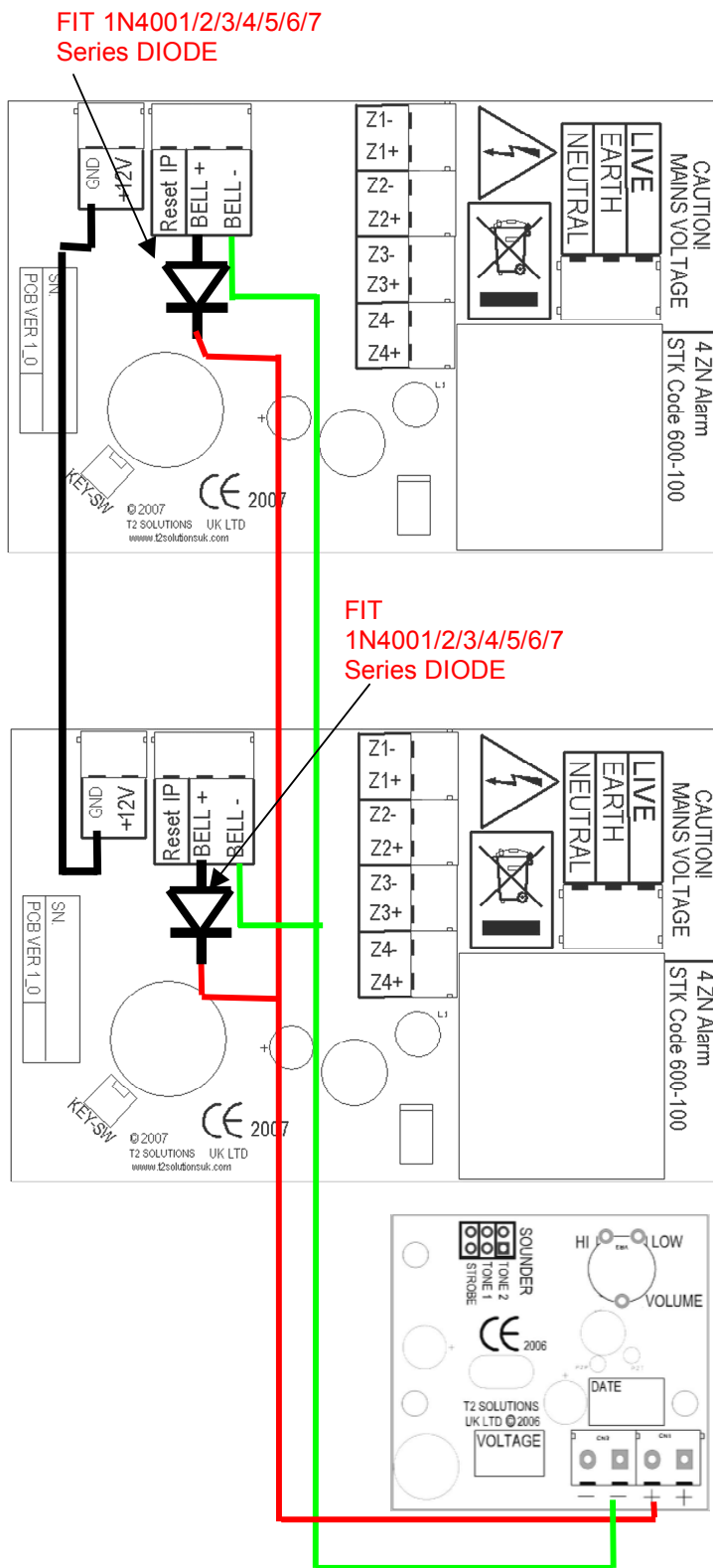

NOTE

The panel GND's must be connected together. DO THIS FIRST.

A Series DIODE must be fitted as shown.

When any panel alarms then all the sounders will operate.